

TP11 due FRI 18 Nov 83

ORG

- 1: Draw a circuit realizing a 4×2 priority encoder
(TEXT Table 11-1 p 439)
- 2,3: Show how to connect 5 4×2 priority encoders
to obtain a 16×4 priority encoder.