

HW #	Problems			due
1	Ch 1	15, 17, 19	Ch 2	9, 10, 11
2	Ch 2	13, 15, 17	Ch 3	21, 23, 33
3	Ch 2	18, 21	Ch 3	5, 22
4	Ch 2	1	Ch 3	26
5	Ch 5	5, 7, 8, 13, 14, 15, 17, 20	Ch 4	10, 11, 12, 18, 25
6	Ch 5	15, 16	Ch 6	11, 12, 13, 22
7	Ch 7	6, 7, 17, 21, 28, 29, 30, 31, 32	Ch 7	1, 2, 9
8	Ch 7	16, 18, 20, 22, 23, 24, 33, 34, 38		
9	Ch 8	2, 5, 8, 10, 21, 24, 25		
10	Ch 9	8, 9	Ch 10	6, 7
11	Ch 11	5, 7, 9, 10, 12, 17, 20, 24, 41, 42, 43	Ch 11	2, 3, 4, 16, 19
12	Ch 12	2, 5, 7, 8, 21, 22, 23, 25, 26		

Test dates

Final: 8pm Wed 11 dec.

Test 1: in class Wed 9 Oct

Test 2: in class Wed 13 Nov.

Bellennot's office hours MWF 1:25- 2:15

218 LOE

usually around most afternoons

TP #	Subject	due
1	1 bit register	4 sept
2	3 bit register	11 sept
3	FIFO buffer 1	18 sept
4	FIFO buffer 2	25 sept
5	Delay circuits	2 Oct test 1
6	Multiplication unit	16 Oct
7	Software Stack pointer	23 Oct
8	Micro Code [& 4 Pg of Notes]	30 Oct
9	Asyn Tx	6 Nov test 2
10	Asyn Rx [& 4 Pg of circuits]	20 Nov
11	Rx Flags	27 Nov
12	Jean's bike	4 dec


1-bit register R.

R has two outputs (Q, \bar{Q}), one input (for load) and four control lines (CLEAR, SET, LOAD, COMPLEMENT).

R satisfies the following table

input	control inputs	current state	next state
	clear set load compl.		
y	0 0 0 0	Q	Q
y	1 0 0 0	Q	0
y	0 1 0 0	Q	1
y	0 0 1 0	Q	y
y	0 0 0 1	Q	\bar{Q}
y	← all others →	Q	? (doesn't matter)

 For example R could be realized using a JK flip flop via the following circuit



YOUR PROBLEM: WITHOUT putting any gates on the clock line NOR using pre-clear or pre-set, realize the 1-bit register R

A. with a D flip flop

B. with a T flip flop

11 Sept
TP 2 due 24 Jan 1985 3-bit register R

R has 6 Outputs $R_2, R_1, R_0, \bar{R}_2, \bar{R}_1, \bar{R}_0$ and 3 inputs y_2, y_1 , and y_0 . There are also control lines for

Load : $R \leftarrow y_2 y_1 y_0$

clear : $R \leftarrow 0$

increment : $R \leftarrow R + 1$

decrement : $R \leftarrow R - 1$

two's complement : $R \leftarrow$ the 2's complement of what is in R

Draw a circuit that realizes the register R subject to the following conditions

1. Use T flip-flops (3)
2. Do not put any gates on the clock line (which can be implicit)
3. Do not use pre-clear or pre-set
4. Do not use any adders (full or half)
5. When all control lines are at 0, the contents of R doesn't change
6. If two or more of the control lines are at 1, we are in a "don't care" mode

Hint: The following algorithm yields the 2's complement of the binary number $b_{n-1} b_{n-2} b_{n-3} \dots b_3 b_2 b_1 b_0$ in an n-bit register.

```
i ← 0
while  $b_i = 0$  do  $i \leftarrow i + 1$ 
i ← i + 1
while  $i \leq n$  do { $b_i \leftarrow \bar{b}_i$ 
                   $i \leftarrow i + 1$ }
```

This algorithm can be done in one clock pulse.

TP 3 & 4 A sort of FIFO buffer designed by two people mad at each other or by a schizoid. X, A, B, C, D, E are registers (n -bits wide, where n is large enuff to avoid overflow in this problem). And a, b, c, d, e are 1 bit flags. The micro-operations controlling this buffer are (note: no timing)

$$\begin{aligned} 1: X &\leftarrow X+1 \\ a'b'c': A &\leftarrow X, a \leftarrow 1 \\ b'c': B &\leftarrow A, b \leftarrow 1 \\ bc': C &\leftarrow B, c \leftarrow 1 \\ cd': D &\leftarrow C, d \leftarrow 1, c \leftarrow 0 \\ de': E &\leftarrow D, e \leftarrow 1, d \leftarrow 0 \end{aligned}$$

TP 3 due ~~31 JAN 85~~ ^{18 sept}


given the μ -operations above and the starting contents below continue filling in the table until all registers but X have stopped changing

starting values	X	A	B	C	D	E	a	b	c	d	e
	20	10	8	6	4	2	0	0	0	0	0
clock pulse per line	{	{	{	{	{	.	{	{	{	{	{

TP 4 due ~~12 FEB 85~~ ^{25 sept}

using RS - flip-flops for the flags a, b, c, d , and e draw a block diagram for this circuit. (ie the control logic that executes these μ -op's)

2 Oct
TP #5 due 21 Feb 85 delay circuits

 


Design two circuits one which takes the given input and produces OUT1. The other takes the given input and produces OUT2.

There are, of course, many ways to do this and what is wanted is a simple solution. The simplest solution is not required. But the ~~more~~ farther your result is from ^{the} simplest ~~solution~~, the farther your grade will be from perfect. Your circuit should not contain "hazards"!

part A. The simplest circuit which from input produces OUT1

part B The simplest circuit which from input produces OUT2

 part C Again the circuit which from input produces OUT1 but this time it must include



In integer multiplication Unit,

$X \& Y$ are 8-bit registers. $T \& PP$ are 16-bit registers

Z is a D flip flop. P is a 1-bit flag. ($P=1$ means

X is a positive 8-bit number, $P=0$ means X is in 2-complement.)

CC (cycle counter) is 3 RS flip-flops which when followed by a 3×8 decoder produces the controls

c_0, c_1, c_2, \dots [reg. numbered from right starting w/ zero]

c_0 : idle

c_1 : not used until part C

c_2 :
 some clock pulse
 $\left\{ \begin{array}{l} PP \leftarrow 0, \\ shr Y Z \text{ (i.e. } Y_7 \leftarrow 0, Z \leftarrow Y_0), \\ \text{if } (P=1) \text{ then } (T(7-0) \leftarrow X \text{ and } T(15-8) \leftarrow 0), \\ \text{if } (P=0) \text{ then } (T(7-0) \leftarrow X \text{ and } T_{15} \leftarrow X_7 \text{ and } T_{14} \leftarrow X_7 \\ \text{and } T_{13} \leftarrow X_7 \text{ and } \dots, T_0 \leftarrow X_7), \\ CC \leftarrow 3 \end{array} \right.$

c_3 :
 some CP
 $\left\{ \begin{array}{l} \text{if } (Z=1) \text{ then } PP \leftarrow PP \oplus T \\ shr Y Z \text{ (} Y_7 \leftarrow 0, Z \leftarrow Y_0) \\ shr T \text{ (} T_0 \leftarrow 0) \\ \text{if } Y=0 \text{ then } CC \leftarrow 4 \end{array} \right.$

c_4 : nothing

- A. Suppose X contains -12 (2-comp), Y contains 5 and $CC=2$ show the contents of each register and each flag in binary after each clock pulse until they stop changing. NOTE $P=0$
- B. Draw a block diagram show all control lines.
- C. This will not work if Y is a negative number in 2's complement but if $Y < 0$ we can multiply both $X \& Y$ by -1. Write down this in Reg Trans lang using c_i .

23 Oct

TP 7 Software Stack Pointer due 28 Feb 85

In Ch7 we have seen several uses for a register used as a "stack pointer" to a stack in memory. However the Ch 5 computer does not have such a register. Your job is to add a stack pointer via software (as in Ch6).

Some storage is reserved to help you

SP :	(the stack pointer)
OLD_AC:	(temp storage for AC)
SUB_ADD:	(temp storage for subroutine address) in call
TEMP :	(additional storage)

Write the routines (SP grows to high memory; AC _{protected})

- A. Pop AC \leftarrow TOS
- B. Push TOS \leftarrow AC
- C. Call TOS \leftarrow PC , PC \leftarrow SUBADD { explain
- D. Return PC \leftarrow TOS
- E. 0-address ADDITION PUSH(POP + POP) (sort of)


using the Ch.6. notation.

DATA FLOW / MICRO CODE (or Hardcore Software)

ORG

Our object is to design a computer that will generate the control for the Chapt. 5 computer.

 1. An Alternate view of the Ch. 5. Computer



We need a total of 24 "control valves" (which are numbered 0 to 23). Once again we can turn this into a control word which we will write in Hex. Examples

020000 just turns on value 17 i.e. $MAR \leftarrow PC$

104000 values 20 & 14 : $MBR \leftarrow M$, $PC \leftarrow PC + 1$

001000 value 12 $IR \leftarrow MBR(OP \& I)$

We have just done a fetch.

To make value 17 work like this is easy. It needs only to select line 17 overline 18 at the input of MAR and put a "1" on the LOAD control for the MAR.

The width of each line differs: Line 10 is 8 bits wide, Line 11 is 16 bits, Line 6 is 16 bits when "7"=1 and 17 bits when "7"=0.

The diamonds contain values: line 0 when selected does $IEN \leftarrow 0$, while line 1 does $IEN \leftarrow 1$,

Not all control words are valid. At most one of "0" or "1" can be selected. Similarly for 16, 19, 20 & 11

2. A very simple computer A CONTROLLER


Our Control Computer has a 7-bit CAR (Control Memory Address register) hooked to a very fast ROM of 2^7 - 25 bit words. It has 1 Output namely the 24 control lines. It has 2 inputs the FLAGS which give the status of the chapter 5 computer and MAP which translates OPCODES of the chapter 5 computer into addresses for the CAR.


Basically it has two instructions: OUT with $CM_{24} = 1$ (CM = Control Memory [CAR]) which just outputs $CM(23,0)$ for control, and a conditional jump $CM_{24} = 0$. This jump takes two forms:

$CM_{23} = 1$ Field $CM(22-19)$ chooses a flag if it is 1
 $CAR \leftarrow CM(13-7)$ otherwise $CAR \leftarrow CM(6-0)$

$CM_{23} = 0$ $CAR \leftarrow MAP$

 in either case all the control lines are zero.



 

FLAG

- 0 MBR ≠ 0 (set if MBR isn't zero)
- 1 FG1
- 2 FGO
- 3 AC(1)
- 4 AC = 0
- 5 E
- 6 Interrupt
- 7 I (indirect bit) and not q₇

MICRO CODE

Pg 4

	00	01	10	11
00000	AND: CW(18)	SKIP: CW(4)	CIA: CW(6,7,8,9)	SZA: CJMP3 SKIP, CHE
00001	CW(20)	CHECK: CJMP(6) RUP, FETC	UJMP CHECK	NU
00010	CW(6,7,9)	FETC: CW(17)	INP: CW(4), 23	NU
00011	UJMP CHECK	CW(20,14)	UJMP CHECK.	NU
00100	ADD: CW(18)	CW(12)	CLE: CW(3)	SZE: CJMP4 SKIP, CHE
00101	CW(20)	CJMP(7) IND, EX	UJMP CHECK	NU
00110	CW(6,9)	EX: JMP MAP	OUT: CW(10), 22	NU
00111	UJMP CHECK	IND: CW(18)	UJMP CHECK	NU
01000	LDA: CW(18,6,7,8,9)	CW(20)	CMA: CW(6,7)	SZE: CJMP5 CHECK, SKP
01001	CIV(20)	JMP MAP	UJMP CHECK	NU
01010	CW(6,9)	RUP: CW(16,13)	SKE: CJMP(2) SKIP, CHECK	NU
01011	UJMP CHECK	CW(17,14)	NU	NU
01100	STA: CW(18)	CW(21,0)	CME: CW(?)	HLT, Blon, Fusc
01101	CW(11)	UJMP FETC	UJMP CHECK	(what should
01110	CW(21)		SKO: CJMP(2) SKIP, CHECK	happen here.
01111	UJMP CHECK		NU	
10000	BUNI: CM(15)		CIR: CW(6,3)	
10001	UJMP CHECK		UJMP CHECK	
10010	NU		ION: CW(0)	
10011	NU		UJMP CHECK	
10100	BSA: CW(18,15,16)		CIL: CW(6,8,9)	
10101	CW(21)		UJMP CHECK	
10110	CW(14)		IOF: CW(1)	
10111	UJMP CHECK		UJMP CHECK	
11000	ISZ: CW(18)		INC: CW(6)	
11001	CW(20)		UJMP CHECK	
11010	CW(5)		NU	
11011	CW(21)		NU	
11100	CJUMP(0) CHECK, SKIP		SPA: CJMP3 CHECK, SKP	
11101			NU	
11110			NU	
11111			NU	

30 Oct

TP 8 due 7 Mar 85 μ-Code

ORG

1. A. Change the micro code on Pg 4 so that STA has op code 9₁ and ADD has op code 9₃
 B. Add the instruction NOP (no operation) with op code I_{9₇}B₁₁ by changing the contents of one address in control memory (which address?)
2. It is decided to replace LSZ with DSZ (decrement and skip if zero). Someone suggested changing value "5" from increment to decrement and not touching the micro-code.
 A. Will this in fact change LSZ to DSZ?
 B. Will this change have any unwanted side effects in terms of the micro control? why or why not?
3. By just changing the content of location 0101001 in control memory and with addition of TFLAG₈ = MBR₁ (leftmost bit) change the computer to allow "infinite" indirection, i.e. if the left most bit is 1 then its address part is a pointer and not the effective address, thus we stay in the indirect cycle until the leftmost bit is 0.
4. Add the figure to right to figure on page 1. If A=1, then MAR \leftarrow (xyz)₂
 i.e. if x=1, y=0, z=1 and A=1 then MAR \leftarrow 5. Also add the values A, x, y & z to our control word.
 Using the micro-code format of page 1 (i.e. CW(11,21))
 A. Write a ~~triple~~ of control words which does "M[3] \leftarrow M[6]"
 B. Write a ~~triple~~ of control words which does "BUN 7" ~~(no indirection)~~ ~~in triple~~
 [you may assume each ~~triple~~ is followed by UJMP Check.]
5. Still using the setting of problem 4 write a sequence of six control words which does "M[0] \leftarrow M[7] + M[4]" (do NOT protect the value in AC).

TP9 due 28 March 85 Asyn Transmitter
(6 Nov)

TX is a 10 bit register with TX_9 connected to a tristate buffer gate which is turned on and off by the RS flip-flop LE (line enabled). The output of the tristate gate is hooked to the LINE (also used in TP's 10 & 11).

TB is 8 bits wide, Count is 4 bits wide and TBE is a flag (RS flip-flop). We have the following μ -ops

$LE' TBE' : \begin{cases} TX_9 \leftarrow 0, TX(8-1) \leftarrow TB, TX_0 \leftarrow 1 \\ LE \leftarrow 1, TBE \leftarrow 1, COUNT \leftarrow 16_{10} \end{cases}$

LE : if count = 0 then (Shl TX, $TX_0 \leftarrow 0$)

LE : if count $\neq 0$ and $TX(8-0) = 0$ then $LE \leftarrow 0$

LE + TBE : count $\leftarrow count - 1$.


Draw a block diagram ~~for~~ circuit that realizes this Transmitter

Show how to modify this circuit so that TX_8 is loaded with an even parity bit instead of TB_7 when $LE' TBE'$

(TBE = transmit buffer empty)
(TX = transmitter)

TP 10 & 11 Asyn Receiver.

The following 4 pages are the same. They show the circuit of an Asyn Rx. Input (Serial) comes from 'LINE'. FGI & INR are as in the Ch.5 computer. There are 4 states

 

TP 10
due
4 Apr
20 Nov

- A. Using the circuit give the μ -ops for each of the states.
 B. In words describe what each state is "doing" and what causes the state transitions.
 Hint: "Color" the active lines a page per state.

TP 11 due 27 Nov
1985 Receiver Flags

We want to add some error flags to our receiver. ER, E/O (even/odd), P/NP (parity/no parity) are control flags. FE (framing error), PE (parity error) and VE (vector overflow error) are status flags. The following μ -op's are added. (ER = error reset) (

$c_2 RR_q' RR_o' : FE \leftarrow 1$

$c_2 RR_q' RR_o' ER : FE \leftarrow 0$

$c_2 RR_q' P : \text{if parity doesn't match, } PE \leftarrow 1$

$c_2 RR_q' ER : \text{if parity match then } PE \leftarrow 0$


$c_2 RR_q' FGI : VE \leftarrow 1$

$c_2 RR_q' FGI' ER : VE \leftarrow 0$

(match means same parity as E/O)

Use RS flip-flops for FE, PE, VE and draw a circuit which does these μ -ops. You have only one 'xor' gate (with as many inputs as you need) and no 'xnor' gates.

CORRECTED 10 Apr 1985

 

15 & 16 Designing a digital bicycle speedometer: The idea is to count revolutions of the front wheel (in rev/sec) and translate this into speed (in mph). The equation $r = 13s$ is helpful, where r = number of revolutions of front wheel per second and s = speed in miles per hour.

A. Assume the register AR contains the number of revolutions in the last second. If speeds of at least 100 mph need to be accurately read, how wide must AR be? _____

B. Assume the register C contains the total number of revolutions since the speedometer was last turned on. If distances of at least 1000 miles need to be accurately reported, how wide must C be? _____

D. To get the correct value in AR from the value in C we add registers OC (old C) and ROC (Real Old C) the same width as AR. Assume the control line p is "1" for exactly 1 clock cycle per second, then the micro-op P: $ROC \leftarrow OC$, $OC \leftarrow C$ (the correct number of low order bits) is done. added to the system. Explain how the value for AR can be obtained.

EFG Draw a block diagram of the system so far (when do you load AR?)


HJ A "look up" table is used to translate the value in AR to the correct output codes to display the current speed. The output display has 3 digits (like 37.2) and each digit is displayed by a 7-segment display unit (decimal point is always on) What size (ie $2^h \times m$) ROM is needed?

JK We are almost done with output, but the display units use too much of the battery and so we need a control line q, which is "1" for exactly 1 clock cycle somewhere between 50 and 100 times a second. The clock rate is 1 Mega Hz and we add another register D with μ-op $1:D \leftarrow D+1$ and let q be the boolean value of ($D=0$). Find the width of D _____ (Values somehow will only be displayed when $D=1$, saving lots of current (i.e. battery juice))

L10N Finally we start on input. A tiny magnet is put on one spoke of the front wheel and a magnetic sensor is placed on the front fork. Spinning the front wheel, we find that the sensor "feels" the magnetic field for $\frac{1}{32}$ of every rotation of the wheel. The clock rate is 1 MHz, how many clock pulses does the sensor "feel" the magnetic field each revolution if the bike is going 100 mph? _____
if the bike is going 1 mph? _____

OP If the sensor sends "logic 1" to the speedometer when it "feels" the magnetic field and "logic 0" otherwise. This input is serially loaded into the register IR which is four bits wide. Label the sensor output line MS (magnetic sensor) write the μ -op which does this and include "control" part in the μ -op.

QRSTUUVWXYZ :

 

Draw a circuit which translates the "leading edge" of M_5 into a 1 clock pulse long output (i.e. so that it's output: $C \leftarrow C + 1$)

Q₁ = 1 → OUT is "1" for one clock cycle then OUT is zero until the next leading edge.

Za: There are 2 states ($Q=0$) and ($Q=1$) describe what each is looking for

($Q=0$):

($Q=1$):

Now we are ready to initialize the speedometer, which of our registers need to be initialized (AR, C, OC, ROC, D, IR) if we don't care if it gives incorrect results speeds or distances for 30secs or so but it needs to be correct after 1 min of operating.

cd How would you initialize the value of C?