

COT 3132 Digital Networks

The good doctor Belletot

TEXT: Kohavi 2nd Ed "Switching & finite automata theory"
off 211 Love
off hrs MWF } 12:30 - 1:00
 } 2:15 - 3:00

GRADES: The classic 90, 80, 70, 60 cut offs
based on

1 Final	30%
3 Tests	45% (15% each)
weekly TP's	15% (See TP sheet)
daily homework	10%

ATTENDANCE is required. Six absences is an automatic fail. A student who does not turn in homework at the beginning of class is considered absent.

HOMEWORK: Only some homework problems are graded. Usually it is all right or all wrong (i.e. no partial credit)

TESTS: In class closed book and closed notes. There will be proofs on the tests.

MATERIAL CHAPT'S 1, 2, 3, 4, 5, 6, 7, 9, 16 and ^{Section} 8.1

TEST PROBLEMS (better known as TP's)

[Note this sheet does not apply to HW.]

1. RULES

- A. They must be on $8\frac{1}{2}$ by 11 paper.
- B. They must be written in ink.
- C. They must use only one side of each page.
- D. If there is more than one page, then the pages must be stapled or paper-clipped together.

Failure to follow any rule costs a point each.

2. Grades

- A. Graded on a 0 to 10 basis.
- B. Graded on your reasoning, your ability to express your reasoning, neatness and your English.

3. Your TP average is computed using only your best n out of the m assigned where $\frac{n}{m}$ is roughly $\frac{2}{3}$.

4. Since TP's are assigned a week in advance of their due date, the solutions handed in are assumed to be carefully worked out. In ANYCASE they will be graded as if they were.

5. They must be your OWN work.

TP2

Digital

due Wed 14 Sept 83

Define the binary operation $|$ (Nand or Sheffer stroke) on any Boolean Algebra by

$$x|y = (xy)'$$

A. (2 points) Show $x|(y|z) \neq (x|y)|z$

B. (2 points) Show $x|x' = 1$ and $x|1 = x'$

C. (6 points) Define $f_0(x) = x$ and for $n \geq 0$ define $f_{n+1}(x) = x|f_n(x)$

Show by induction that for $n \geq 1$

$$f_n(x) = \begin{cases} x' & \text{if } n \text{ is odd} \\ 1 & \text{if } n \text{ is even} \end{cases}$$

TP1 induction $a_n = (a_{n-1})^2 \Rightarrow a_n = 2^{2^n} \quad a_0 = 2$

TP3 realize $x', x+y, x \cdot y, x \oplus y, xy + x'y'$ by NANDS ALONE } few gates
 & NORs ALONE } as possible

The basic circuit of TTL (Transistor-Transistor Logic) is the NAND gate (which can have more than two inputs.)

The basic circuit of ECL (Emitter-Coupled Logic) is the NOR gate.



In each case, you need ~~not~~ no other gates since all other gates can be obtained from NAND gates alone or NOR gates alone. { This property is called functionally complete }

Your problem is to construct circuits that realize the given function (switching function) using NAND gates alone and then using NOR gates alone. Only unprime inputs x, y, z are available. Your answer should use as few gates as possible. You may use gates with more than two inputs

A. $f(x) = x'$ B. $f(x, y) = x + y$ C. $f(x, y) = xy$
 D. $f(x, y) = (xy)'$ E. $f(x, y) = (x + y)'$ F. $f(x, y) = x \oplus y$
 G. $f(x, y, z) = x \oplus y \oplus z$ H. $f(x, y, z) = xy + yz + xz$

(Note G & H worth twice A, B, C, D, E and F (ie 2 pts ea vs 1))

Make your circuits NEAT

  


Complete the timing diagram if all gates

- A. Have a delay of zero n.s.
- B. Have a delay of one n.s.
- C. Have a delay of two n.s.
- D. Have a delay of three n.s.

Design and realize a 2-bit binary multiplication unit.


(Your circuit ~~show~~ is to meet the standards below like the half-adder show.) I.E. you have 4 inputs $x_1, x_0, y_1, & y_0$ and 4 outputs $m_3, m_2, m_1, & m_0$ so that
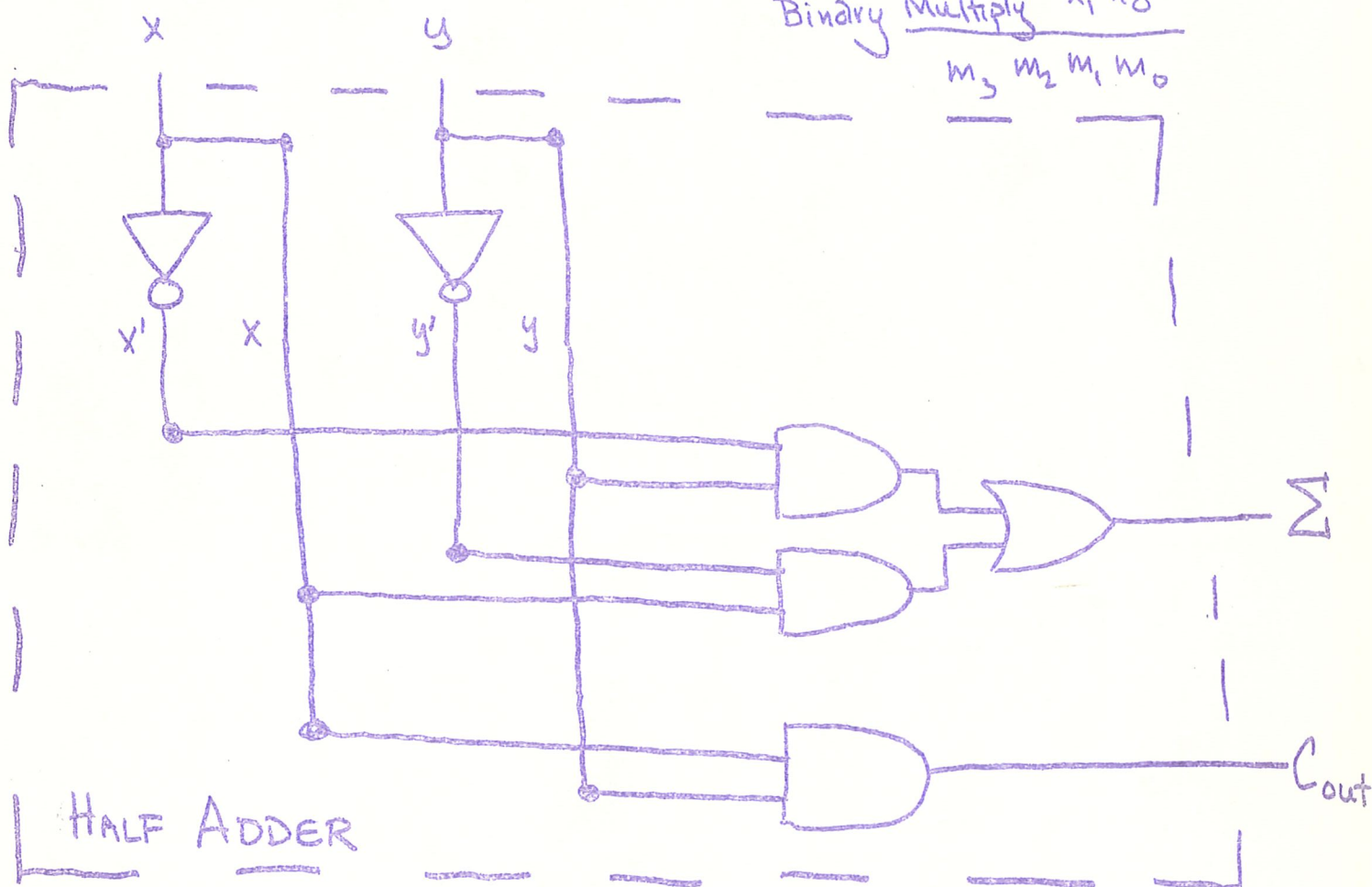
$$\begin{array}{r} y_1 y_0 \\ x_1 x_0 \\ \hline m_3 m_2 m_1 m_0 \end{array}$$




1. EACH OUTPUT IN MINIMAL SUM OF PRODUCTS
2. ALL LINES HORIZONTAL OR VERTICAL
3. NO "JUMPS" OR "HOOPS"
4. INPUTS AVAILIABLE ONLY "ONCE" AND ONLY UNPRIMED

TP6 PART A DIGITAL

 


TP 6 PART B DIGITAL

 

TP 7 due Mon 24 OCT 83


digital.

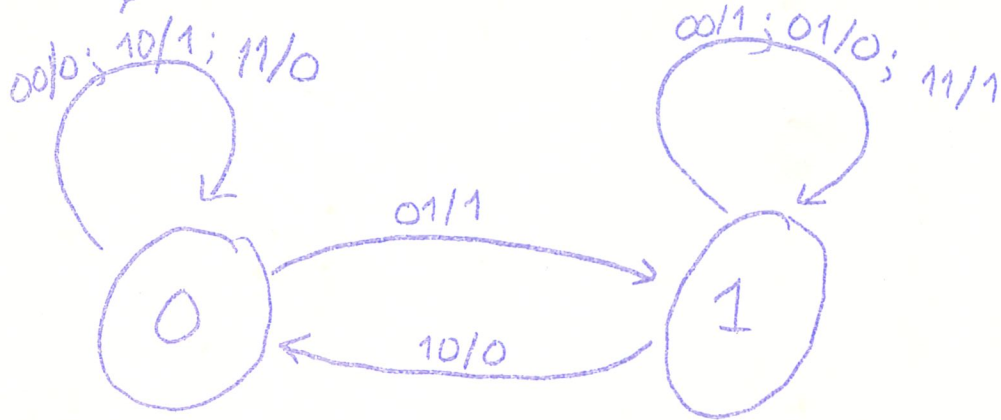Use a T flip-flop to realize the following state diagram
(inputs xy/z output)



B is state variable

 
and complete the following diagram (T is neg. edge triggered)



An Arithmetic circuit has two "selection variables" or "controls" S_1 & S_0 together with C [carry in] so that

S_1	S_0	$C = 0$	$C = 1$
0	0	$A + B$	$A + B + 1$
0	1	A	$A + 1$
1	0	\overline{B}	$\overline{B} + 1$
1	1	$A + \overline{B}$	$A + \overline{B} + 1$

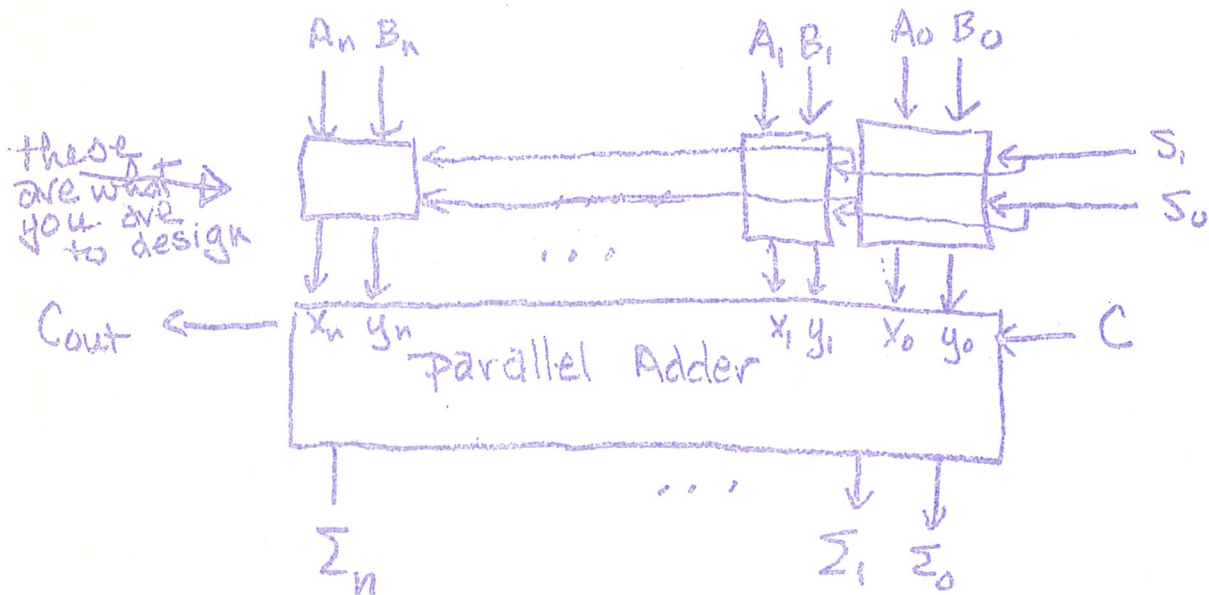
(Here $\overline{B} = B'$) (And + is addition)



Determine the circuit (and draw it) that must be incorporated with a full adder in each stage of the arithmetic unit to produce the desired outputs above.

Design and realize a 3-bit counting register X made from three T-flip-flops with controls E (enable), L (load), C (count), U/ \bar{D} (if 1 going up, if 0 going down). It has three inputs I_2, I_1, I_0

E	L	C	U/ \bar{D}	Current state			Next state		
				X_2	X_1	X_0			
0	ϕ	ϕ	ϕ	Q_2	Q_1	Q_0	Q_2	Q_1	Q_0
1	0	0	ϕ	Q_2	Q_1	Q_0	Q_2	Q_1	Q_0
1	1	ϕ	ϕ	Q_2	Q_1	Q_0	I_2	I_1	I_0
1	0	1	1	Q_2	Q_1	Q_0	R_2	R_1	R_0 (Clockwise)
1	0	1	0	Q_2	Q_1	Q_0	S_2	S_1	S_0 (CounterClockwise)

 

↻ direction counting up

↻ direction counting down

TP 11 due Wed 23 Nov 83

digital

Use an RS flip-flop to design a DE-unit

DE	current	next		
0 0	Q	Q	← E=0	HOLD
1 1	Q	Y	← E=1	LOAD

and use three of them to realize the shift register below

$C_2 C_1 C_0$	CURRENT	NEXT	
0 0 0	$Q_2 Q_1 Q_0$	$Q_2 Q_1 Q_0$	HOLD
0 0 1	$Q_2 Q_1 Q_0$	$I_2 I_1 I_0$	LOAD (I_j inputs)
0 1 0	$Q_2 Q_1 Q_0$	$Q_1 Q_0 I_0$	SHIFT LFT w/LOAD
0 1 1	$Q_2 Q_1 Q_0$	$Q_0 Q_1 Q_2$	REVERSE
1 0 0	$Q_2 Q_1 Q_0$	$Q_2 Q_2 Q_1$	ARITH SHIFT RT
1 0 1	$Q_2 Q_1 Q_0$	$Q_0 Q_2 Q_1$	ROTATE RT
1 1 0	$Q_2 Q_1 Q_0$	$0 Q_2 Q_1$	SHIFT RT w/ZERO FILL
1 1 1	$Q_2 Q_1 Q_0$	$Q_2 Q_0 I_0$	ARITH SHIFT LFT w/LOAD

USE A 3x8 DECODER w INPUTS $C_2 C_1 C_0$ TO GET "CONTROL LINES"

TP 12 Use 5 4x2 priority encoders to make 16x4.