

## Digital Practice Test (PT 1.)

1. Two 8-bit registers have  $(8C)_{16}$  and  $(F9)_{16}$  resp. has contents what is the outcome in hexadecimal if they are "XOR"ed?
2. Define "single error detecting codes" and state what is meant by minimal product of sums form of a switching function
3. Simplify the boolean alg exprs  $x+y'+(x+y'+z)'$  &  $xy+(x+z)'y'$
4. Show in any boolean alg  $a \leq b \Leftrightarrow a \leq c \Rightarrow b \leq c$   $\left[ a \leq b \Leftrightarrow a \cdot b = 0 \right]$
5. Proof that NAND<sup>3</sup> is functionally complete
6. Draw a map for the function  $f(x,y,z)$



7. For  $\sum m_0, m_2 = (0, 2, 4, 5, 6, 8, 10, 12)$  find all the prime implicants which are essential? Give a minimal sum of products form for f. Is it unique?

8. Prove or disprove  $xy + x'y + x'z + yz = xy + xy' + x'z + yz$

9.  $f(w,x,y,z) = \sum (0, 2, 4, 9, 12, 15) + \sum p (1, 5, 7, 10)$   
AB give a min sum of prod.  
CD give a min sum of prod.  
E1 is the ones in A3 unique?  
E2 is the ones in C3 unique?  
E3 which is minimal (neither, AB, CD, or both)

10. Show that  $f(x,y,z) = (x+y)z'$  is functionally complete

11. Show for any boolean alg  $x \oplus (yz) = (xy) \oplus z$  and  $x \oplus (x \oplus y) = y$

12. Prove by induction for  $n \geq 2$  (in any boolean alg)

$$x \oplus x \oplus \dots \oplus x = \begin{cases} 0 & \text{if } n \text{ is even} \\ x & \text{if } n \text{ is odd} \end{cases}$$

13. Give a minimal two level AND-OR realization of the function in #6 above

14. Explain why the following yields a min prod of sums form for f

1. Map f
2. Complement the map
3. Find min sum of prod form for the new map
4. Complement ans in 3
15. Will the code 0110, 1001, 1111, 1100, 0011 detect single errors? why or why not?
16. For any boolean alg define  $A \otimes B = B + A'$   
prove or disprove  $A \triangleright B = B \triangleright A$ .

TP 9 Due Nov 23

1-bit register R.


R has two outputs ( $Q, \bar{Q}$ ), one input (for load) and four control lines (CLEAR, SET, LOAD, COMPLEMENT). R satisfies the following table

control inputs	input	clear	set	load	compl.	current state	next state
Y	0	0	0	0	0	Q	Q
Y	1	0	0	0	0	Q	0
Y	0	1	0	0	0	Q	1
Y	0	0	1	0	0	Q	1
Y	0	0	0	1	0	Q	?
Y	0	0	0	0	1	Q	?
Y	0	0	0	0	0	$\bar{Q}$	?

↳ all others  $\rightarrow Q = ?$  (doesn't matter)

For example R could be realized using a JK flip flop via the following circuit

input

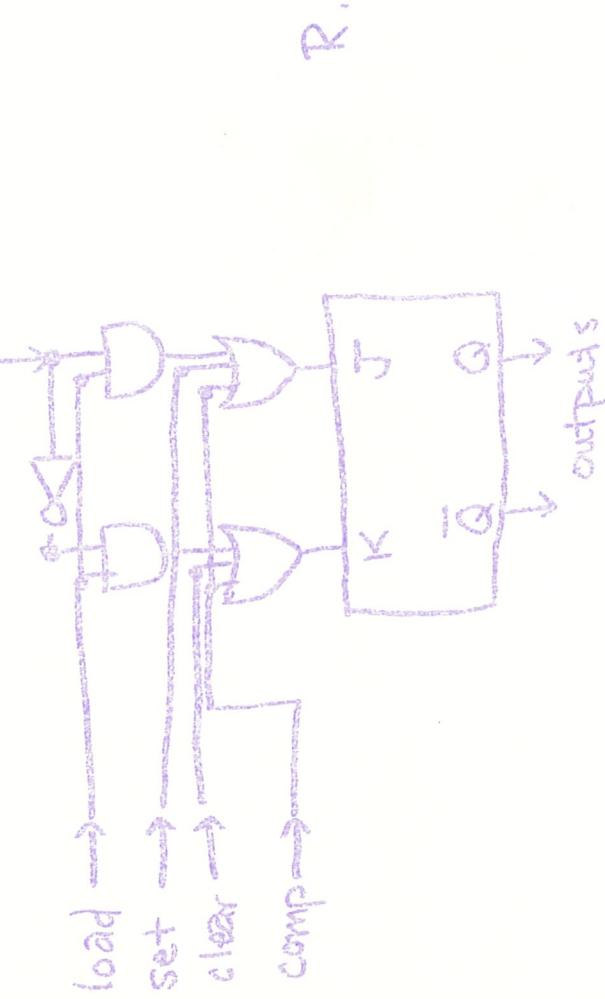

YOUR PROBLEM: WITHOUT putting any gates on the clock line NOR using Pre-clear or Preset, realize the 4-bit register R


A. with a D flip flop

B. with a T flip flop

digital

TP 6 due: Mon 17 Oct 63


digital

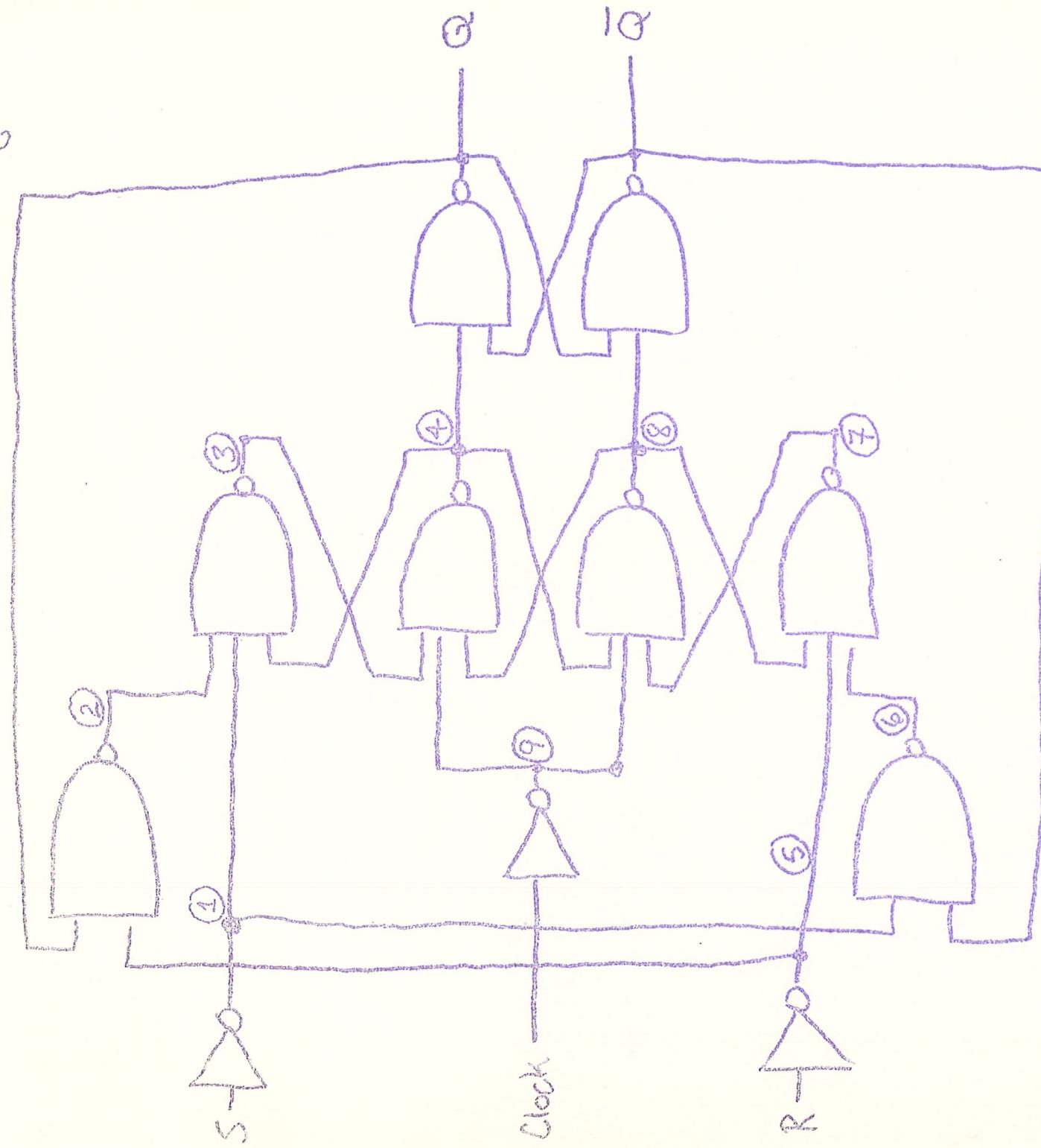

ALL GATES HAVE DELAY OF ONE ns

initially
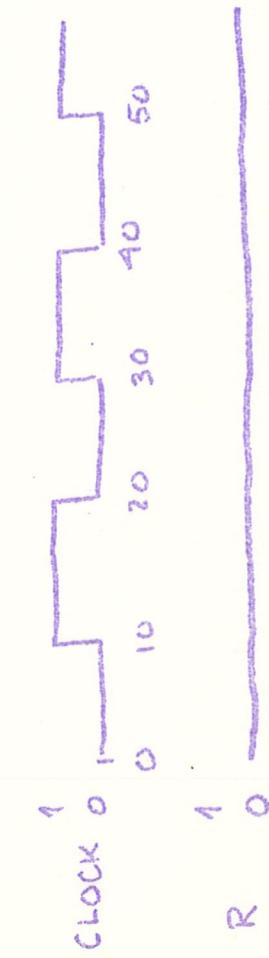
$$\begin{aligned} R &= S = \text{CLOCK} = Q = \bar{Q} = 0 \\ 1 &= 5 = 7 = \bar{Q} = 2 = 4 = 0 \end{aligned}$$




DO TIMING DIAGRAMS FOR BOTH CHOICES OF INPUT S








digitized

4.1

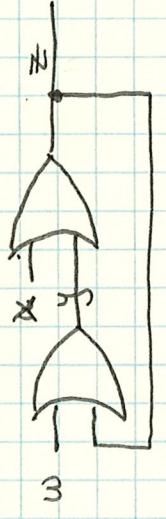


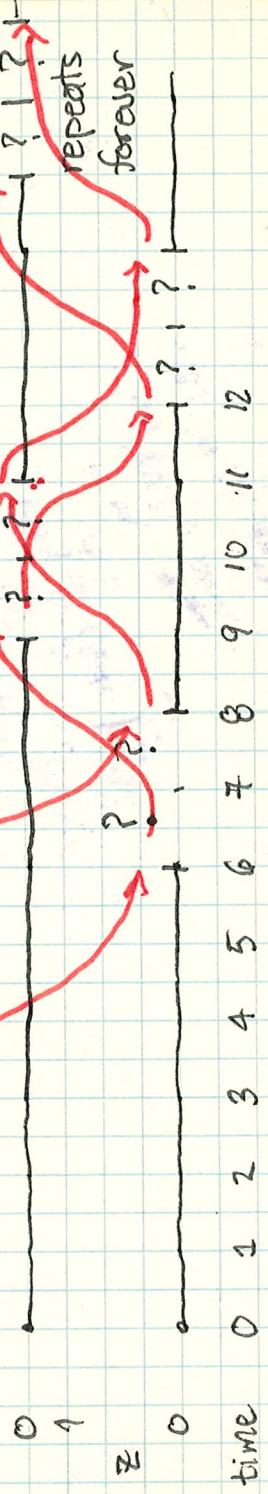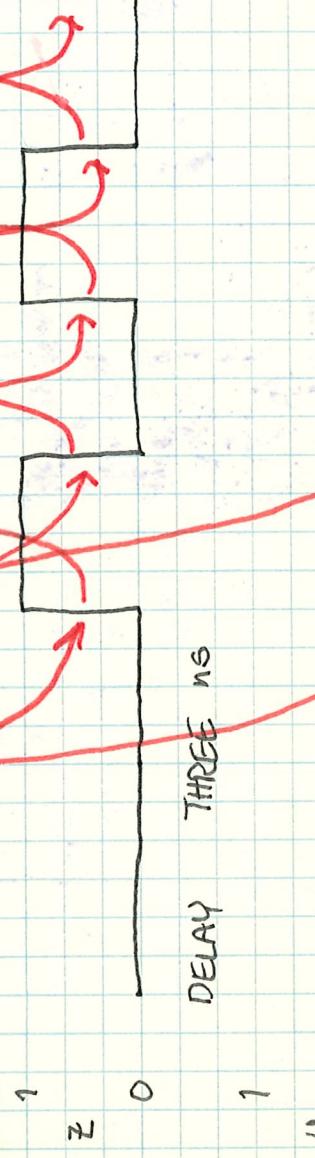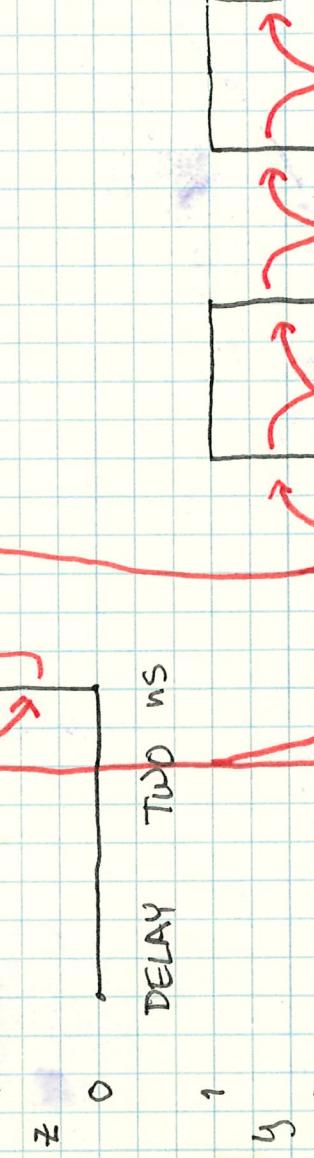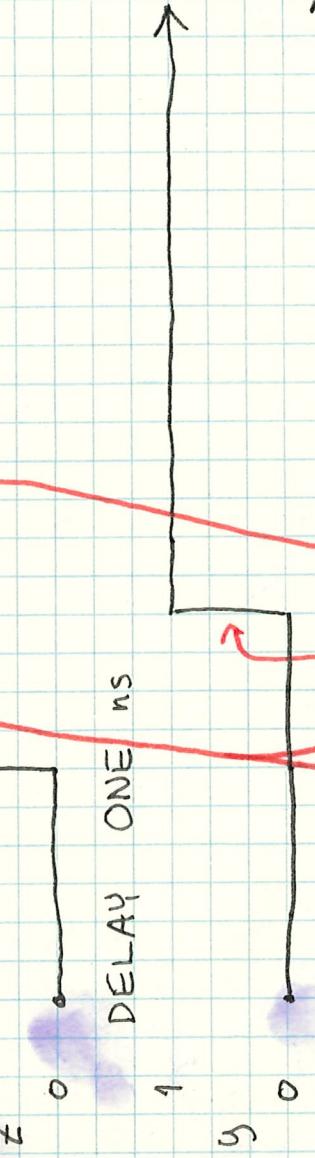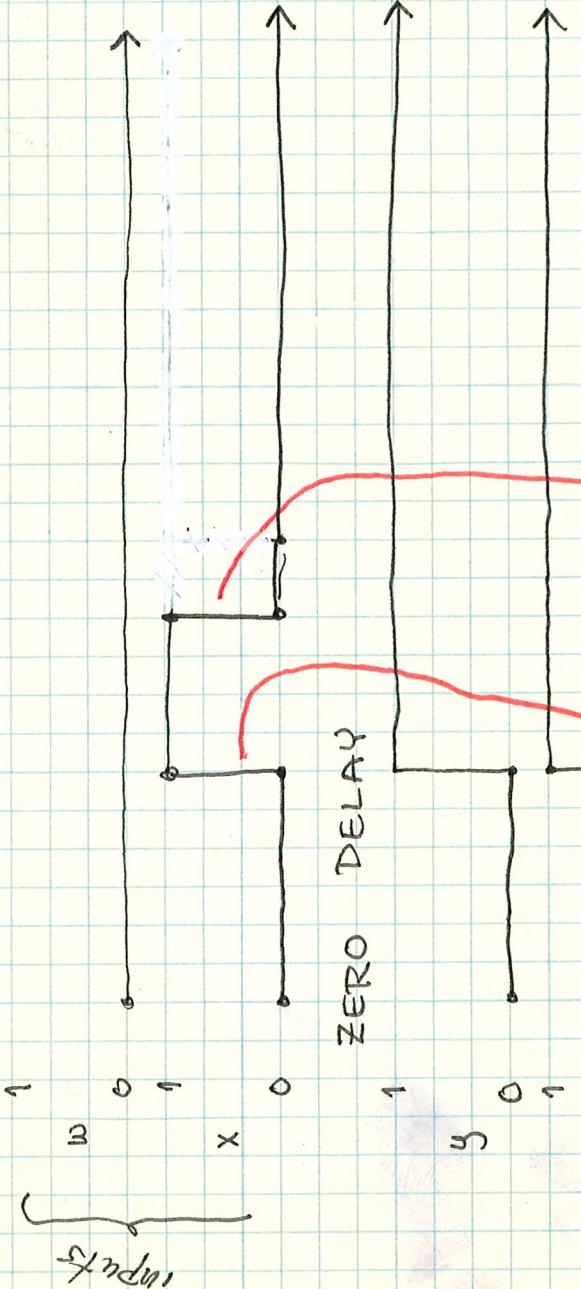time 0 1 2 3 4 5 6 7 8 9 10 11 12 (in Nano Secs)



4.2

## TUT 2

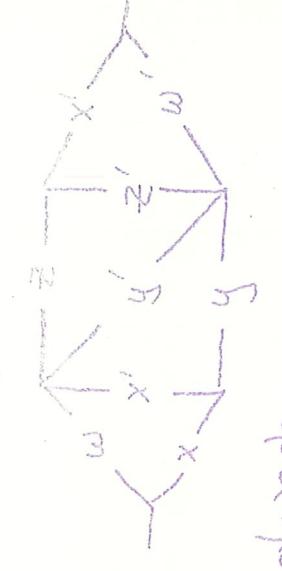

1. A. Find all the tie sets & cutsets for the contact network to right.  
 B. Give a map of the function  
 C. Find an equivalent series parallel network.
2. Assuming there is at most one error in the Hamming code 1110010  
 A. Circle the bit in error or say there is none. B. decode the message.  
 C. Encode "5" in Hamming code



3. Give a map for the threshold unit to right  
 B Use our technique for map entered variables  
 On the map to right:
- A. Use 3 2x4 decoders with enable to make a 3x8 decoder with enable

B. Use a 3x8 decoder and an or gate to realize  $f(x, y, z) = x \oplus y \oplus z$

C. Do the same for port (B) with a 8x1 multiplexer

5. Give a state diagram which will recognize the sequence 010 (overlaps ok) i.e if input  $y = 1000101001001010100001$  then output is  $z = 00000101001000100001$

6. do a time diagram for all gates have a delay of 1 ns.



$$A = 0 \quad B = C = D = 1 \quad \text{initially}$$

7. Realize the state table using a JK flip flop

8. List the need excitations

9. for prime implicant chart  
 A. Which implicants are essential?

- B. Which implicants are in every minimal express


- C. Which implicants are in no minimal express.

10. Realize  $f = xy$  using only nand gates, using only nor gates.

11. Give a state table for the circuit to right


12. Assuming there is at most one error in the Hamming code 1110010  
 A. Circle the bit in error or say there is none. B. decode the message.

- C. Encode "5" in Hamming code

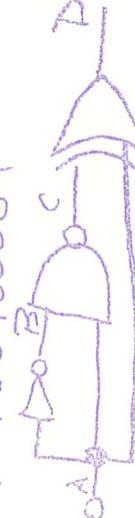


	$x=0$	$x=1$
$y=0$	0/1	1/0
$y=1$	1/1	0/1

	$x=0$	$x=1$
$y=0$	0 to 0	1 to 1
$y=1$	1 to 0	0 to 1

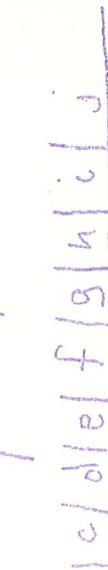

### TS DIGITAL

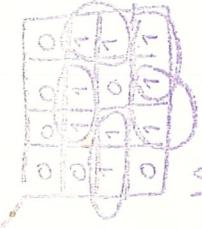
1. Find all static hazards in the map  
partition and a state table in standard form for reduced



2. Carefully step by step construct the equivalence partition and a state table in standard form for

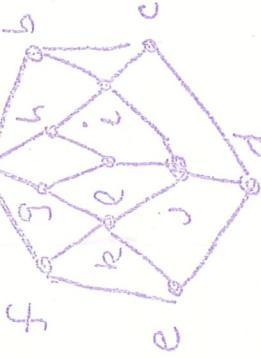3. A. Find All the complements of e in the Hasse diagram

$$\begin{aligned} \text{B. If } x = 101010, y = 100111 \\ \text{then } q_b \text{ of } x \in y \text{ is } \underline{\quad} \\ \text{and } q_u \text{ of } x \in y \text{ is } \underline{\quad} \\ \text{(register order)} \end{aligned}$$



4. For each of the relations on  $N = \{0, 1, 2, 3, \dots\}$  and properties below either say yes or say no and give a counterexample  
 $x R y$  iff  $|x - y| \leq 3$ ;  $x S y$  iff  $x \leq y + 3$   
 A. is it reflexive B is it symmetric C is it anti-symmetric  
 D. is it transitive E is it irreflexive

5. Use full (half) adders and a decoder to realize  $S_{0,4,6}(x, x_2 x_3 \dots x_7)$   
 6. Write  $A' S'_{1,2,3}(B, C, D, E) + A' S'_{2,3,4}(B', C', D', E')$  as a symmetric function of  $A, B, C, D, E$  using the "S" notation

7. A. Design a set-dominant unit using a TS flip-flop

B. Use a set-dominant unit to realize a JK flip-flop

C. Design a unit using an RS flip-flop such that the 11 input is a hold otherwise it is the same as a TS flip-flop

8. The function  $f(v, w, x, y, z) = \sum(8, 10, 13, 24, 28) + \sum_x(v, w, x, y, z, 27, 31)$  has a decomposition of the form  $F(w, z, \overline{D}(v, \underline{y}))$ . Find it.



9. A. Design  $S_{0,1,2}(w, x, y, z)$  using a contact network with a minimum of contacts  
 B. Realize this same function using one threshold unit

10. Use contact networks with minimum of springs to realize  $T(w, x, y, z) = \sum(6, 9, 11, 14, 15)$  [12 springs] Partial credit for circuits with more springs if # of springs stated.

11. the circuit Start of D op to right is a ring counter. initially Start = 1. What is the next state?  
 After the first clock pulse Start = 0; list the states which follow in their order.

12. Use two flip flops and a decoder to produce the same output sequence as  $Q_3 Q_2 Q_1 Q_0$  (i.e. draw the circuit)  
 12. List all possible reduced state tables in standard form with 2 or less states, where the output is always 0 when current state is A and always 1 when the current state is B

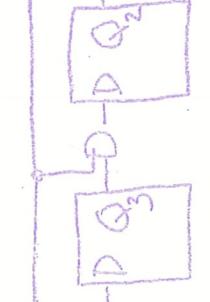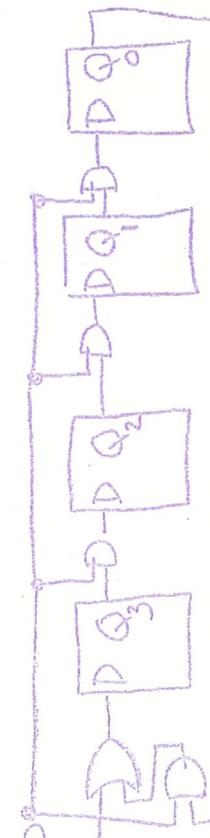13. Design a 4-bit register with controls  $c_0, c_1$  s.t. when  $c_0 = c_1 = 0$  it holds, when  $c_0 = 1, c_1 = 0$  it counts up & when  $c_0 = 0, c_1 = 1$  it counts by twos.



## Simplification Test

S.S.no.

Shoafali Dorte for Credit 1-4 : 10pts ea 5-8 15 pts ea.

A. "Or" the two 8-bit registers containing  $(A_3)_{16}$  and  $(A_7)_{16}$  and express the outcome in hex decimal

B. Define a single error detection code:

2. Prove or disprove:  $x'z + yz + xy = x'z + yz + xz$  (Any BooleanAlg)




3. Prove for any boolean algebra  $xy + [(x'z)'(w'y + z')]' = xy + x'z$

A. Show  $f(x,y,z) = (x+y')z'$  is functionally complete

5.A.  $f(w,x,y,z) = w'x'y' + x'y'z' + y'z'$  realize f as a two level circuit using only AND or OR gates. (primed variables available)

B. Draw a map for  $f$  in part A.  
  
 $= \overline{w} \overline{x} \overline{y} \overline{z} \quad 01 \quad 11 \quad 10$

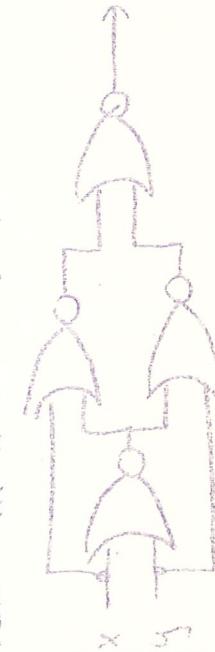C. Write the output of the circuit below in a sum of products form




### SIGNAL

test three


by \_\_\_\_\_ Show all work for credit 1-4 10 pts each 5-8 15 pts each

1. A. Indicate All static hazards in the circuit to the right in the map beside it.

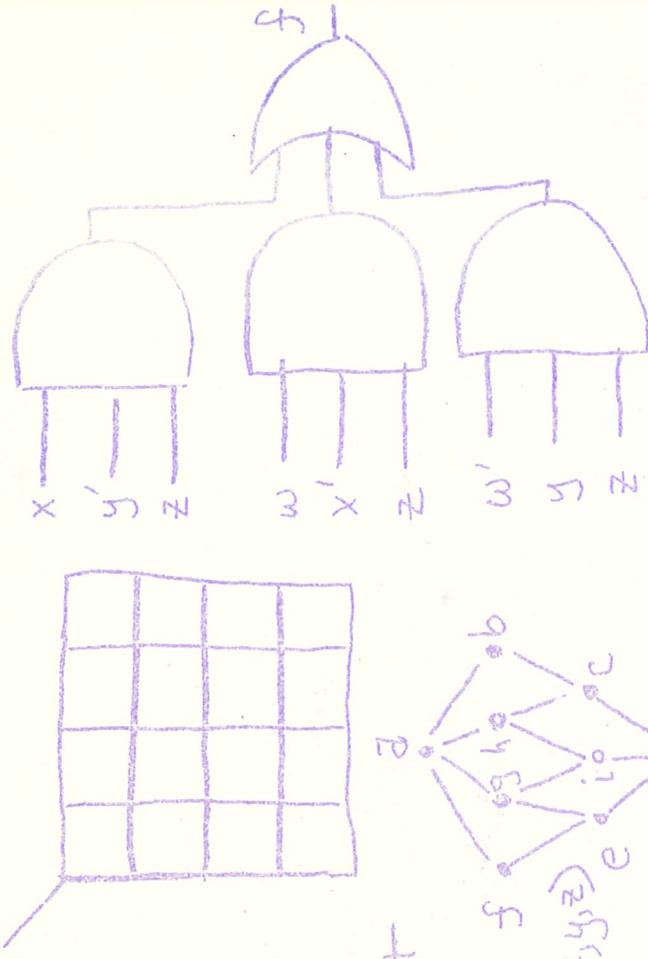- B. List All complements to e in the Hasse diagram to the right



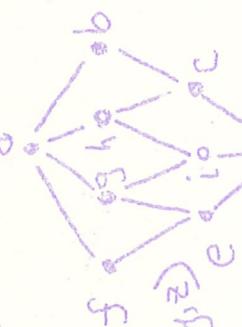2. The function  $f(y, w, x, y, z) = \sum(1, 15, 20, 21, 27) + \sum_{\phi}(4, 10, 11, 19, 26)$  has a decomposition of the form  $F(w, y, \Phi(x, y, z))$ . Find it.



3. The relation  $R$  is defined on  $\{1, 2, 3, \dots\}$  by  $x R y \iff x$  divides  $2y$  with no remainder. For each property below either claim  $R$  has that property or claim  $R$  does not have that property and give an example to show it doesn't

- A. Reflexive

- B. Symmetric

- C. Antisymmetric

- D. Transitive

4. The function  $AB S_3(C, D, E) + A B' S_0(C, D, E) + A' S_2^{'} S_4(B, C, D, E) + A' S_2^{'} S_4(B, C, D, E)$  is a symmetric function of  $A, B, C, D, E$ . Write it using the  $S$  notation

5. A. Rewrite the state table to right in standard form


	$x=0$	$x=1$
A	C/0	A/0
B	A/0	B/1
C	C/1	D/0
D	A/1	B/1

BCD Carefully "Step by Step" construct the equivalence partition for the state table to the right. Show ALL work.

	$x=0$	$x=1$
A	C/0	E/0
B	D/1	F/1
C	E/0	G/0
D	F/1	H/1
E	G/0	I/0
F	H/1	B/1
G	G/0	B/0
H	B/1	D/1

E. Give a minimal length sequence that distinguishes state C from State E.

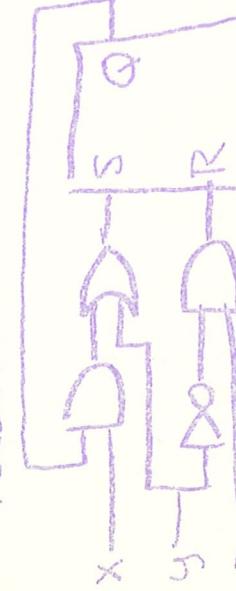6. AB. Fill in the action column of the table to right for the circuit below. HOLD, SET, CLEAR, COMPLEMENT AND FORBIDDEN are "ACTIONS"



$\times \quad u \quad z \quad | \quad \text{ACTION}$

0 0 0	
0 0 1	

0 1 0	
0 1 1	

1 0 0	
1 0 1	

1 1 0	
1 1 1	

$S, S_0$	ACTION
0 0	HOLDS
0 1	COMPLEMENTS
1 0	SETS
1 1	CLEAR

↑  
A

↑  
B

↑  
C

↑  
D


J	Q	Q
K		

3	2	1	0
$S_1$	$S_0$	$Q$	$\bar{Q}$

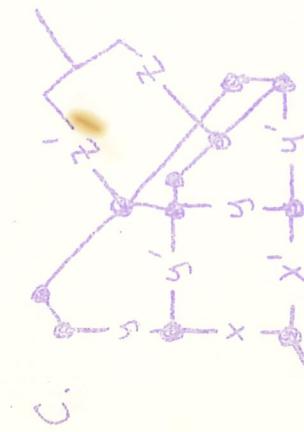7. Simplify the following contact networks

$$\text{A. } \left[ \begin{array}{c} x' - w' - y - z' \\ x - w - y' - z \end{array} \right] \\ (\text{12 springs})$$

$$\text{B. } \left[ \begin{array}{c} w - b \\ x - d \\ c - a \\ z - y \end{array} \right] \\ (\text{7 contacts})$$



(2pts for 8 springs  
more for less)

8. Using the T-flip flops below and the control line  $C_1$  to realize a circuit which does  $\rightarrow$
- | $C_1$ | Current State     | Next State         |
|-------|-------------------|--------------------|
| 0     | $Q_3 Q_2 Q_1 Q_0$ | $Q_3' Q_2 Q_1 Q_0$ |
| 1     | $Q_3 Q_2 Q_1 Q_0$ | $P_3 P_2 P_1 Q_0$  |
- Where  $\{Q_i\}$  if  $Q_{i-1} Q_{i-2} \dots Q_0$  are all zero  
 $P_i = \{Q_i\}$  otherwise (i.e. if there is a one anywhere to the right)

Control Line  $C$

$$\left[ \begin{array}{c} T_3 \\ T_2 \\ T_1 \end{array} \right] \quad \left[ \begin{array}{c} Q_3 \\ Q_2 \\ Q_1 \end{array} \right] \quad \left[ \begin{array}{c} \overline{Q}_3 \\ \overline{Q}_2 \\ \overline{Q}_1 \end{array} \right]$$


$$\left[ \begin{array}{c} T_2 \\ T_1 \end{array} \right] \quad \left[ \begin{array}{c} Q \\ \overline{Q} \end{array} \right]$$

$$\left[ \begin{array}{c} T_0 \\ Q_0 \end{array} \right] \quad \left[ \begin{array}{c} \overline{Q}_0 \end{array} \right]$$

$$\left[ \begin{array}{c} T_0 \end{array} \right] \quad \left[ \begin{array}{c} Q_0 \\ \overline{Q}_0 \end{array} \right]$$

Q. 1. Encoder by 4 bits & 8 bits for credit 4-4 worth 15 pts

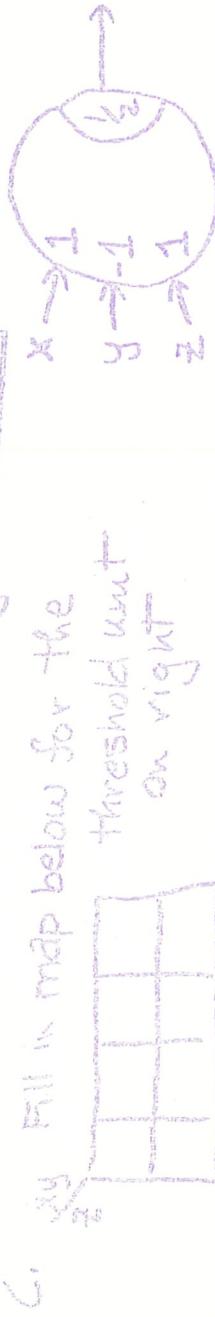4. The Hamming Code is used to send a decimal number and the following was received:  
A. Assuming at most one error either CIRCLE the bit in error above or SAY there is no error  
B. What is the decoded message?




2. For the contact network to right

A. List all tie sets

B. List all cut sets


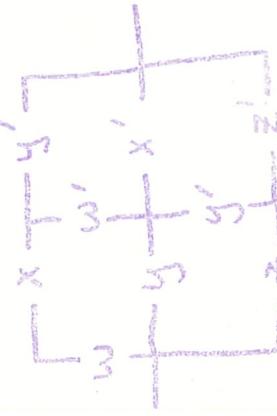
3. CAREFULLY showing ALL work use the TABULATION method to find all prime implicants of  $f(x,y,z) = \Sigma(3,4,5,6,7)$   
Do NOT construct a prime implicant chart.



4. Realize the function  $g(x,y,z) = \Sigma(3,5,6,7)$  using


A. The decoder & another gate B. The multiplexer

8x1  
multiplexer

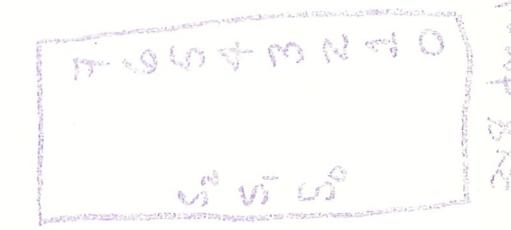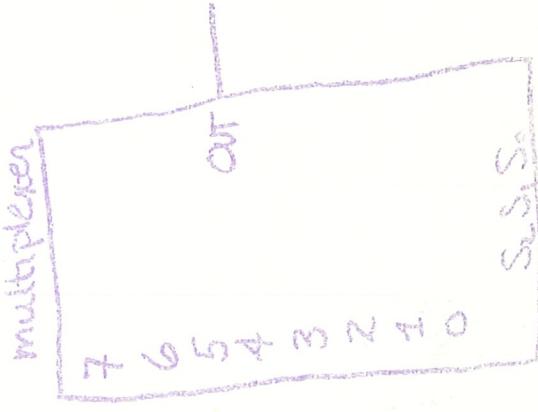

3x8 decoder

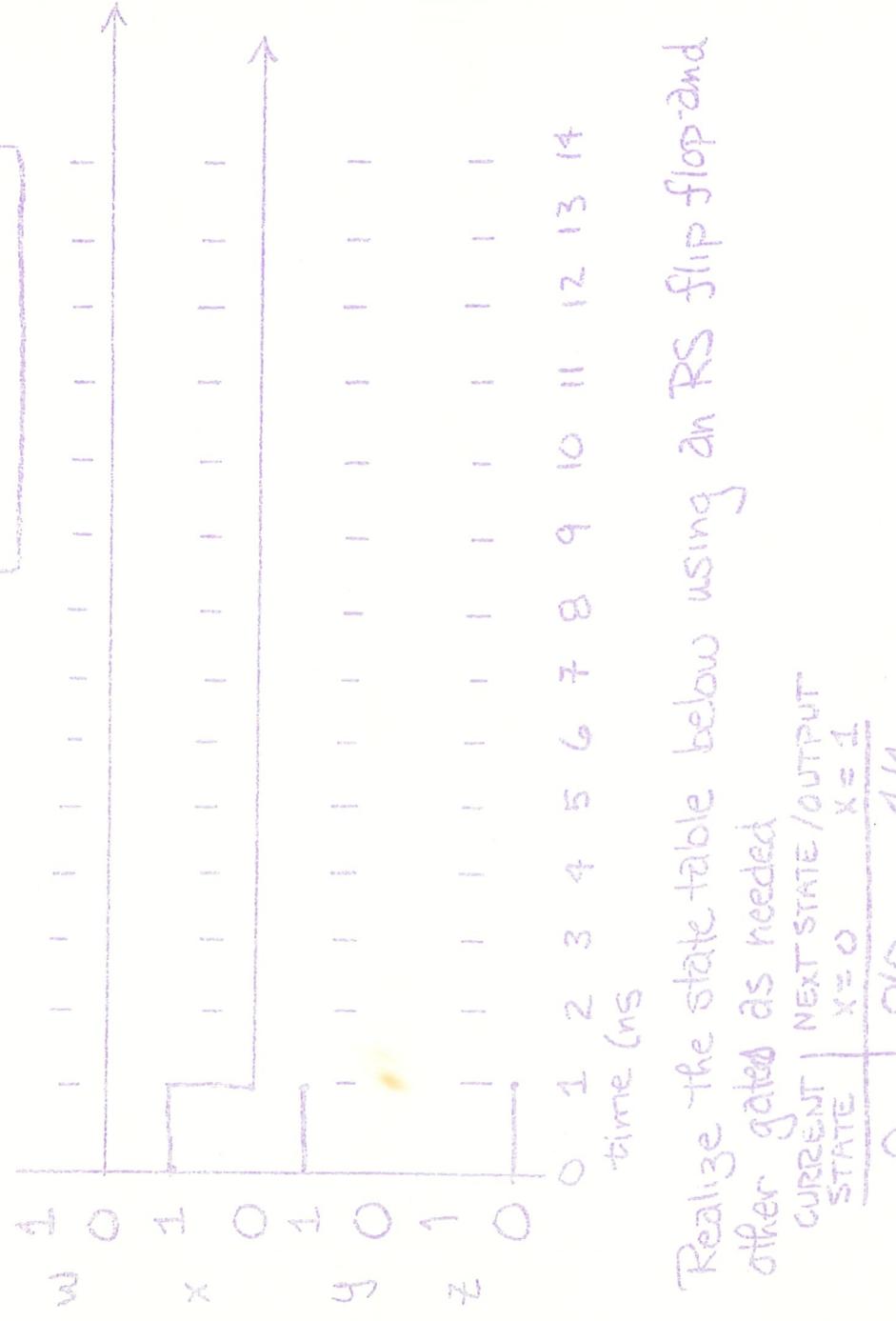
5. Complete the timing diagram below. Both gates have a delay of one nanosecond. Be sure to include ARROWS



6. Realize the state table below using an RS flip-flop and other gates as needed

CURRENT STATE	NEXT STATE / OUTPUT
0	0/0
1	0/1

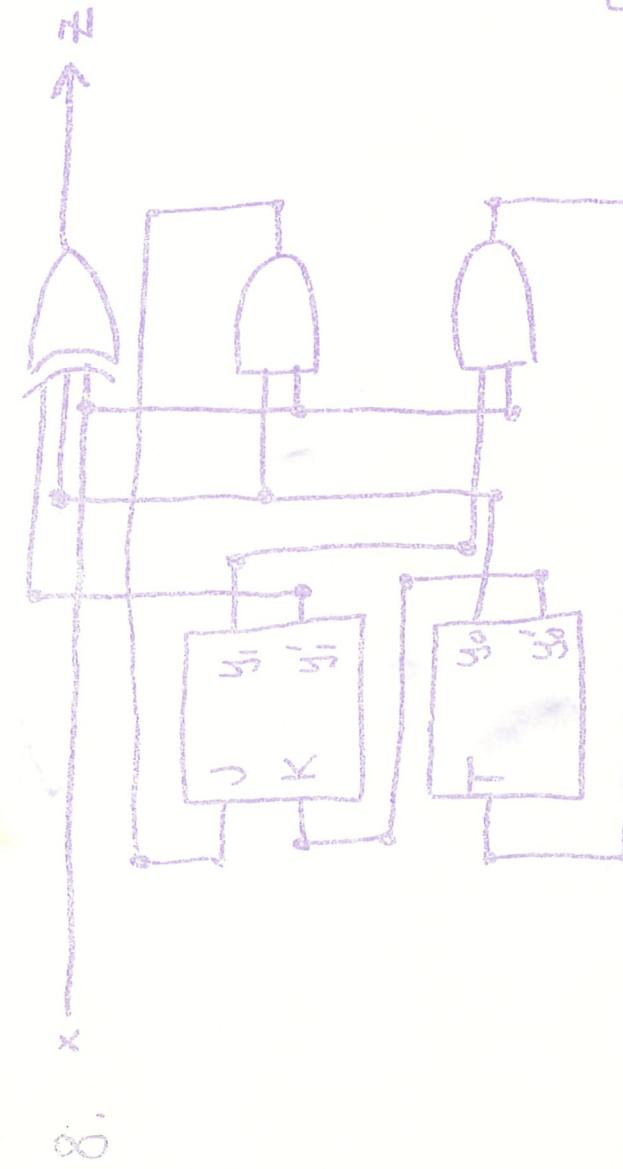Q. Given a state diagram which will recognize the sequence  $000$  and the sequence  $11$  (overlaps o.k) i.e if  $x = 0010000111$  clearly label which state you start in then  $z = 0000011011$



Flip Flops are triggered on negative edge


A. Complete the state table below

CURRENT STATE $y_1y_0$	NEXT STATE / OUTPUT $x = 0$	$x = 1$
00		
01		
10		
11		

B. Suppose  $X$  is always 1 complete the following  
clock      [ ]      [ ]      [ ]  
Y1      1      0      1  
Y0      0      1      0  
Z      0      1      0

- A. Give the working principle of changes in which direction  
 CHANGES  
 $\begin{array}{l} \text{O to O} \\ \text{O to A} \\ \text{A to O} \\ \text{A to A} \end{array}$
- B. Trace numbered arrows with map symbols

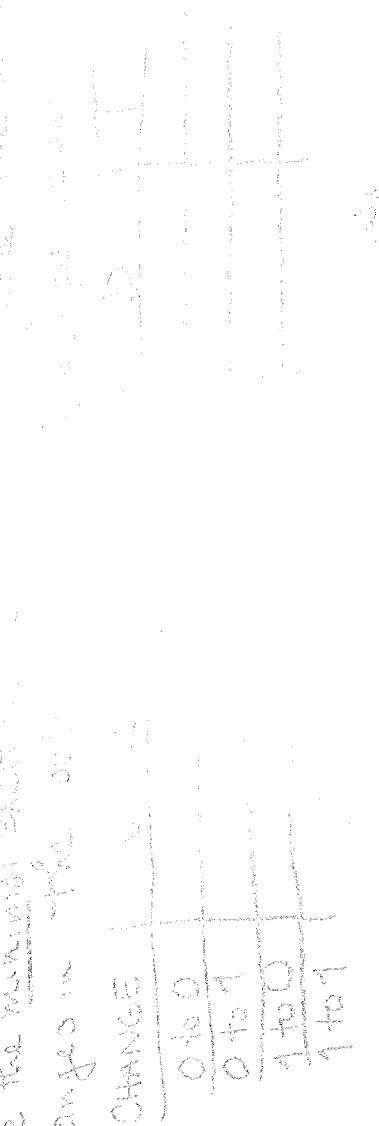C. Give the working principle of changes in which direction



D. Using one or more functions  
 Assume length of string  
 m

B. Write the code for the base class

A. Find out what is the output of the following program?

B. Give all the odd numbers from 1 to 100.

C. Find out what is the output of the following program?

D. Find out what is the output of the following program?

P2


6. The relation  $R$  on  $\{0, 1, 2, 3, \dots\}$  is defined by  
 $x R y$  if and only if  $|x - y| \leq 3$ . Answer yes or no  
and if no give an example which shows why  
A. is  $R$  reflexive?  
B. is  $R$  anti-symmetric?

C. is  $R$  symmetric?  
D. is  $R$  transitive?

7. Show for ANY boolean algebra  $x \oplus (x \oplus y) = y$   
 $(x \oplus y = xy' + x'y)$

8. Show that  $f(x, y, z) = (x \wedge y) \oplus z'$  is functionally complete

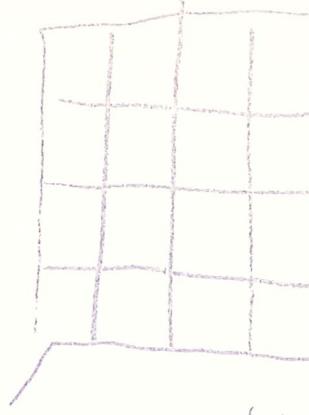9.  $f(w, x, y, z) = \sum_i (0, 2, 4, 9, 12, 15) + \sum_\phi (1, 5, 7, 10)$   
AB. give a minimal sum of products form for  $f$ .



- CD. give a minimal product of sums form for  $f$

- E1: Is your answer in AB unique? (yes/no)  
E2: " " " " CD unique? " "  
E3: Which of these two cases do you think is more likely?


10. Draw a transition graph for concepts  $\overline{1}(11+0)^* \overline{1}(11)^*(00)^* \overline{1}$

a. Use full adders (halves or 3/4) and other things to realize  $S_{0,4,6}(x_1, x_2, \dots, x_7)$


b. Use a decoder

12. Complete the timing

diagram:  
 $t=0$      $w=x=y=z=0$   
the input  $x$  &  $y$  change as below  
(arrows need to show what causes what)  
All DELAYS = 1ns

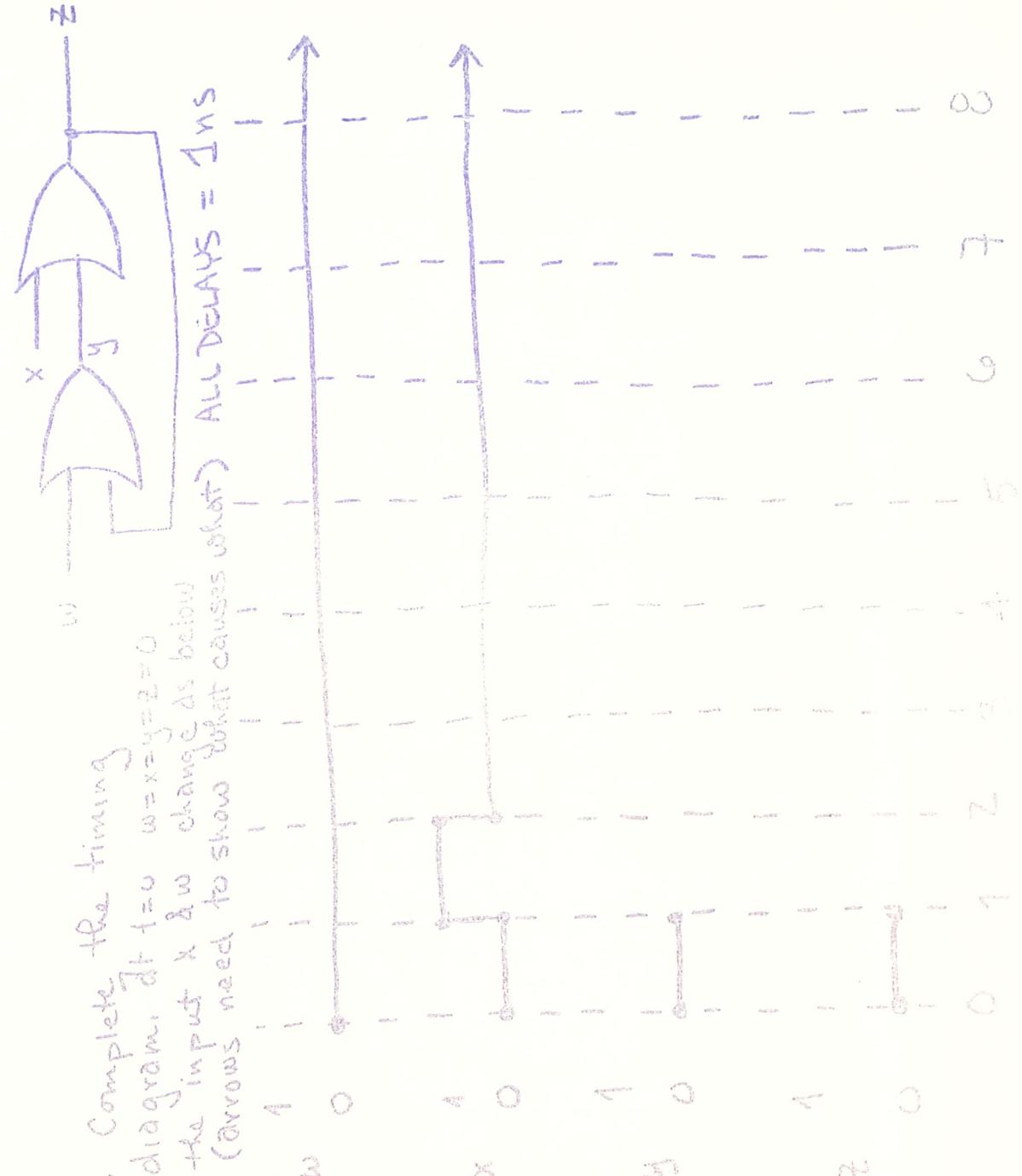

Pg 4

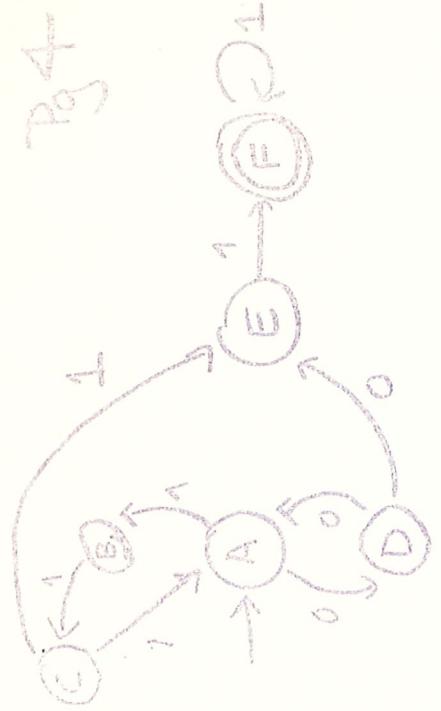

13. For the transition graph

A. write a regular expression for the sequences accepted by it

B. Give a state table for an equivalent deterministic machine.

Current State	Next state/output
y	x = 1
0	0/0

14. Realize the state table to right using a RS flip-flop and some gates

15. Design a way to hook up the inputs  $x_i$  to any of the output  $z_j$



$x_3$  —  
 $x_2$  —  
 $x_1$  —  
 $x_0$  —

telephone line  
 (anks is Ma Bell)

$C, C_0$  i.e.  $C_0 = 10 \cdot S_1 \cdot S_2 \cdot 0 \cdot 1$   
 Control

$x_3$  —  
 $x_2$  —  
 $x_1$  —  
 $x_0$  —


telephone line  
 (anks is Ma Bell)

$C, C_0$  i.e.  $C_0 = 10 \cdot S_1 \cdot S_2 \cdot 0 \cdot 1$   
 Control

16. The finite state machines A & B are physical, ie. A has  $n$  flip-flops and B m flip flops plus some other gates.

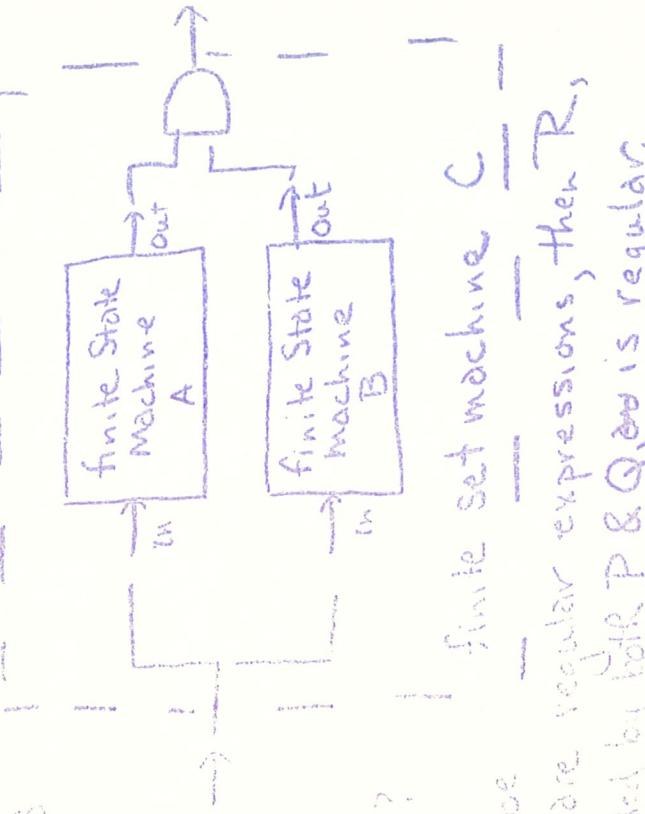A. What is the most number of states machine C can have?

B.C.D.E. Explain how this can be used to prove if P and Q are regular expressions, then  $R$ , the set of sequences accepted by both P & Q, is regular.



3132 bytes done

Show all work for Credit. 10pts each

Good luck


1. If  $x = \begin{pmatrix} 1 & 0 & 1 & 0 & 1 & 0 \end{pmatrix}$  and  $y = \begin{pmatrix} 1 & 0 & 0 & 1 & 1 & 1 \end{pmatrix}$

then A. all 6 of  $x \wedge y$  is 1  
and B. all 6 of  $x \vee y$  is 1

C. Assume there is at most one error in the Hamming code.

D. circle the bit in error or say there is none.

D. What is the missing?

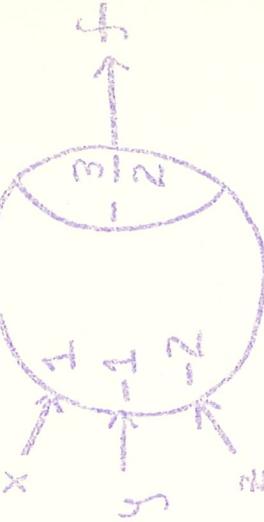

2. A. Fill in the map  $\pi_{\text{odd}}$  for the function given by the threshold unit to right

B. Realize the map in 2A with a series-parallel network.

C. circle the bit in error or say there is none.

D. What is the missing?

	$\pi$	$\sigma$	$\phi$	$\psi$	$\chi$	$\psi$	$\chi$	$\pi$	$\sigma$	$\phi$	$\psi$	$\chi$	$\psi$	$\chi$	$\pi$	$\sigma$	$\phi$	$\psi$	$\chi$
A	X																		
B		X																	
C			X																
D				X															
E					X														
F						X													
G							X												
H								X											
I									X										
J										X									
K											X								
L												X							
M													X						
N														X					
O															X				
P																X			
Q																	X		
R																		X	
S																			X

3. For the prime implicant chart

to right, implicants A, B, C have one less literal than DEF,G.

A which implicants are essential?

B. which non-essential implicants are in minimal expression? E

C. which implicants are G never used?

D. The relation R on the sets  $\{A, B, C, D, E, F, G, H, I, J, K, L, M, N, O, P, Q, S\}$  is defined by  $(x, y) \in R \iff x \neq y \text{ and } \text{rank}(x) \leq \text{rank}(y)$ . Decide yes or no to the following

E. Is R reflexive?

F. Is R anti-symmetric?

G. Is R transitive?

Q. 1. XOR the two 8-bit registers containing  $(A3)_{16}$  and  $(47)_{16}$  and express the outcome in hexadecimal.

B. For the same register pairs express their g.l.b. in hexadecimal.

C. A. Encode 6 into Hamming code

B. The function  $S_2(345)(xyz)$  can be realized using one threshold unit. Do it.

3. A. Use our technique for map entered variables to find a minimal expression for the map  $\rightarrow$

B. Use this 8x1 multiplexer to realize this map.

0	1	2	3	4	5	6	7
$S_2$	$S_1$	$S_0$					

A. For the contact network to right

A. List all tie sets

B. List all cut sets

$x$	$y$	$z$	$w$	$u$	$v$	$x'$	$y'$	$z'$	$w'$	$u'$	$v'$
0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	1	1	1	1	1	1	1	1

5. The function  $AS_{02}(B',C',D',E') + A'S_{124}(B,C,D,E)$  is a symmetric function of  $A,B,C,D,E$ . Write it using the S notation.


6. The relation  $R$  is defined on  $\{1, 2, 3, \dots\}$  by  $xRy \Leftrightarrow x-y=3$ . For each property below either state  $R$  has that property OR state that it doesn't have the property and give an example to show it doesn't. A. Reflexive | B. Symmetric | C. Antisymmetric | D. Transitive

4. Show  $f(x,y,z) = x' + yz'$  is functionally complete


8. Give a state diagram which recognizes the sequences  
 $001, 0001, 00001, \dots, \underbrace{0 \dots 0}_{\text{two or more zeros}}, 1, \dots$
- Clearly label your starting state

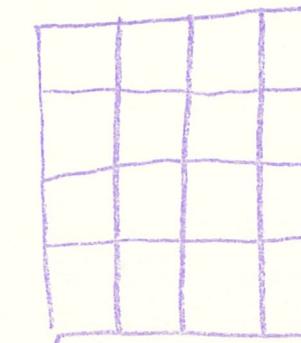9. For  $f(w,x,y,z) = \sum (0,2,4,6,7,10) + \sum (3,5,8,15)$

AB Find all minimal sum of products expressions for f



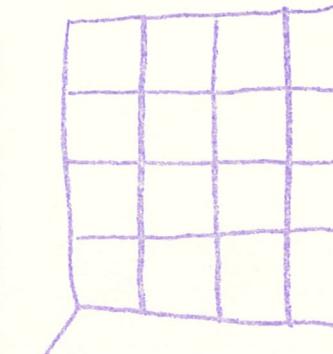CD Find all minimal product of sums expressions for f



E. Which are minimal overall?

10. Define or state what it means  
 A. Symmetric function  $f(x,y,z)$

- B. Irreflexive relation R on  $\overline{X}$

- C. the sup of  $x \notin y$



Use 5  $2 \times 4$  decodes with enable (like one below) inside the box to realize the Ax16 decoder shown




$S_3$   
 $S_2$   
 $S_1$   
 $S_0$



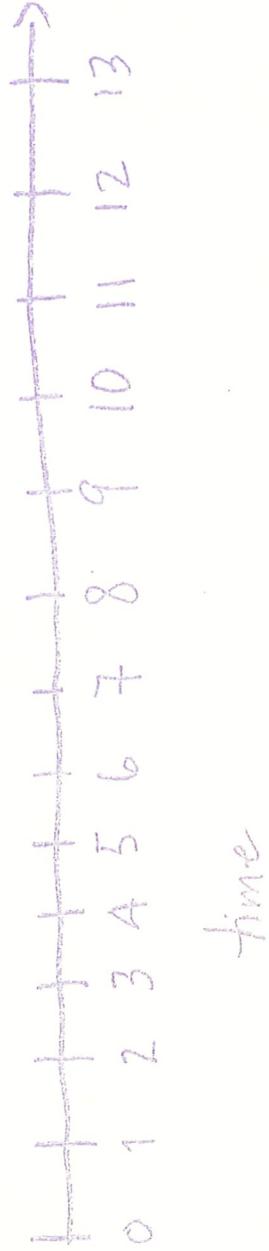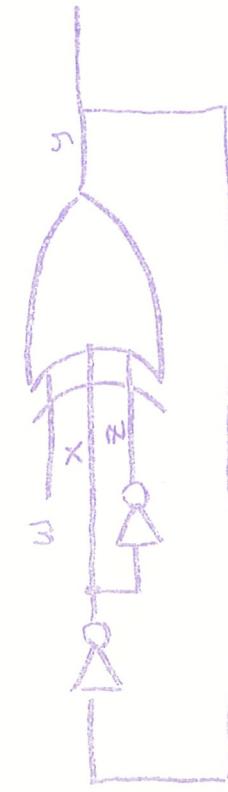12. Complete the timing diagram below. All gates have 4 ns delay  
ARROWS are required



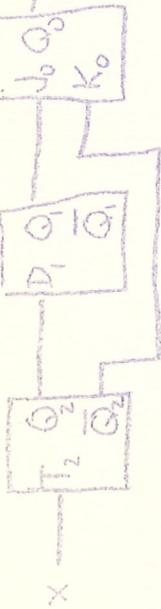Q<sub>2</sub>, Q<sub>1</sub>, Q<sub>0</sub>: Fill in the state table for the circuit below



B Complete the following assuming the input X is always 1

CLOCK	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Z
0	0	0	0	0
1	1	0	0	1
2	0	1	0	0
3	1	1	1	1
4	0	0	1	0
5	1	0	1	1
6	0	1	1	0
7	1	1	0	1
8	0	0	0	0

14 Realize the state table below using two JK flip flops and as few gates as possible.

Q <sub>1</sub> Q <sub>0</sub>	X = 0	X = 1
00	11/0	10/0
01	01/0	10/0
11	10/1	00/1
10	11/0	00/0

Help  
of  
X=0

15 Prove or Disprove. (For Any Boolean Algebra)

A.  $xy + x'z = [(x'+y')(x+z')(yz)']'$

B.  $x'y + xz + x'z = yz + x'z + y'z + x'y'z' + xy + x'y'z'$

16. Prove by INDUCTION: No matter which state you start in, after the input sequence for  $n \geq 0$

$$1101 \quad 0001 \quad 0001 \quad \dots \quad 0001$$

$\underbrace{\hspace{1cm}}$   
n repetitions

	$x=0$	$x=1$
A	D/I/O	A/I/O
B	A/I/O	A/I/O
C	B/I/O	A/I/O
D	D/I/O	C/I

the current output is 1 and the next state is C